




Ohm's Law


By
Alemneh Assefa

Questions to Investigate

- What is the relationship between electric current and voltage?

Ammeter reading & Range

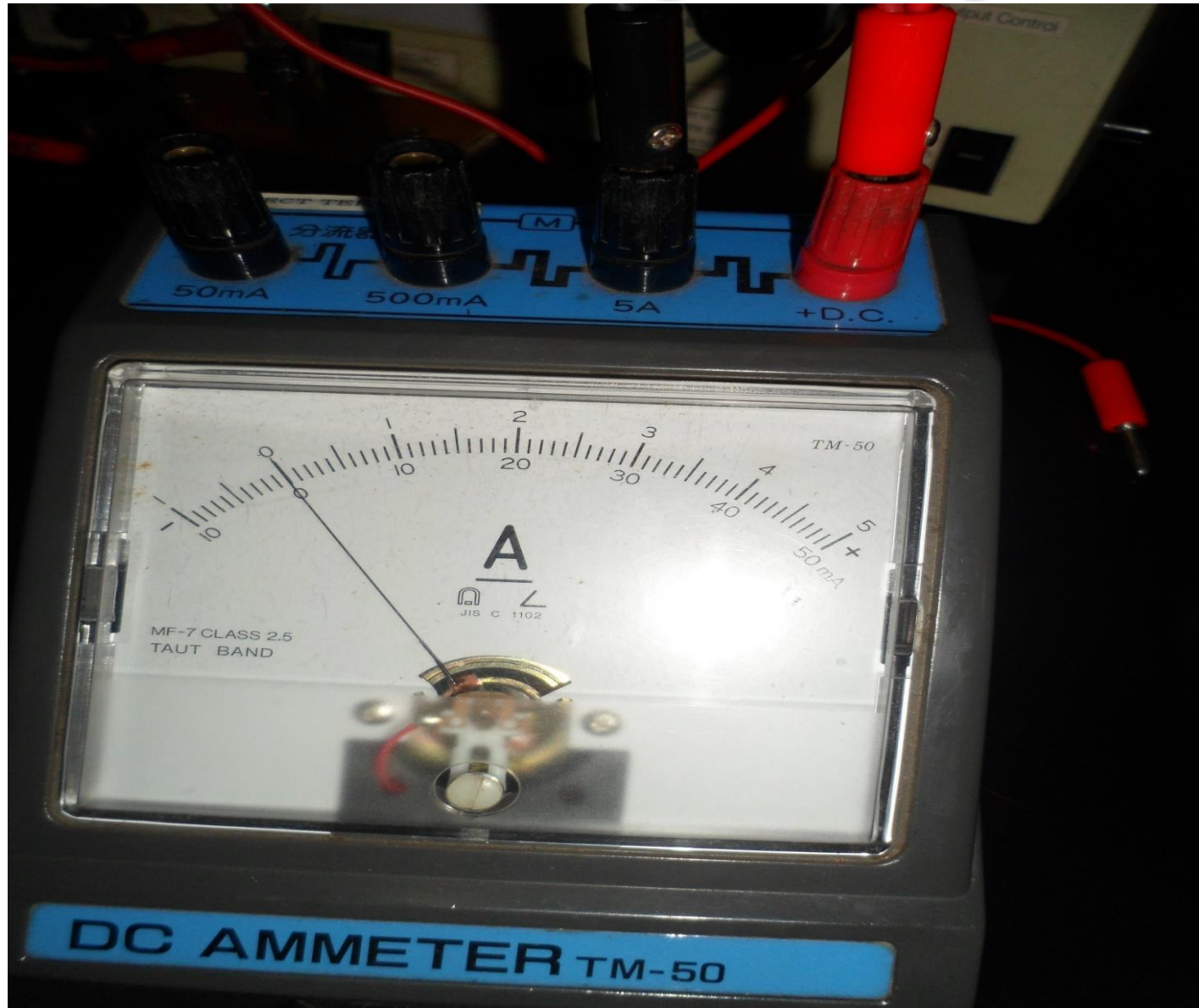

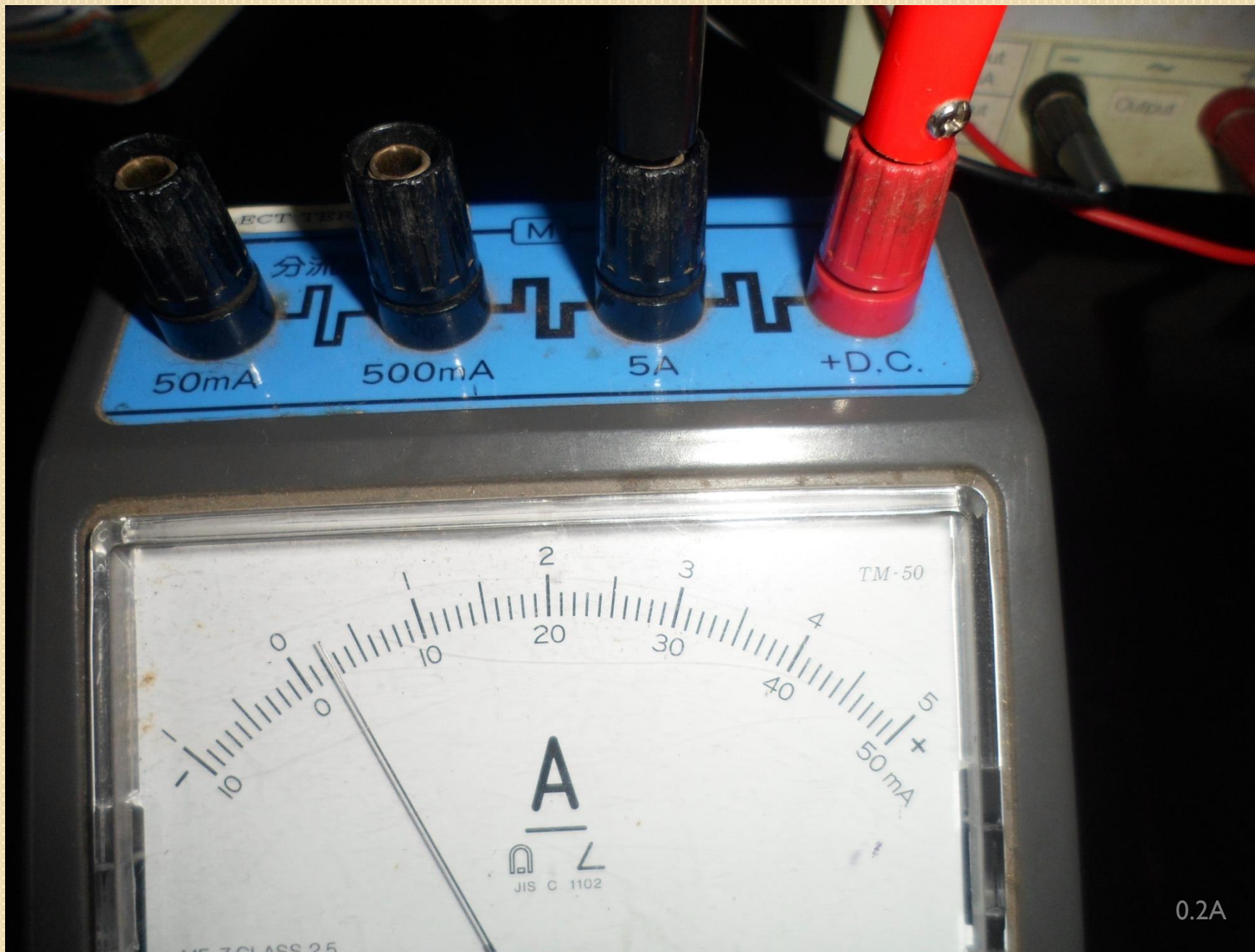


0.2A




1.3A

Voltmeter Reading & Range

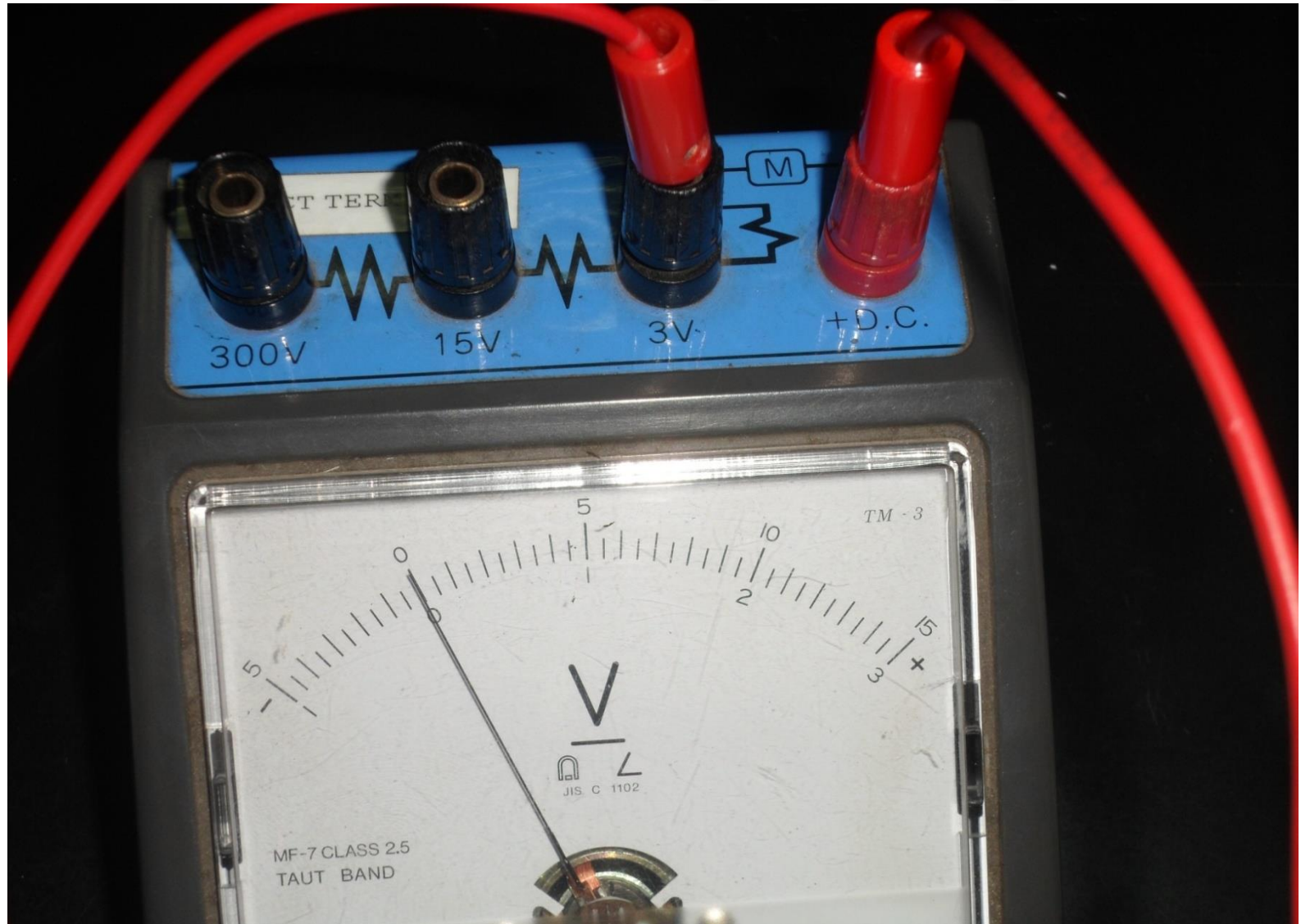


0.4V

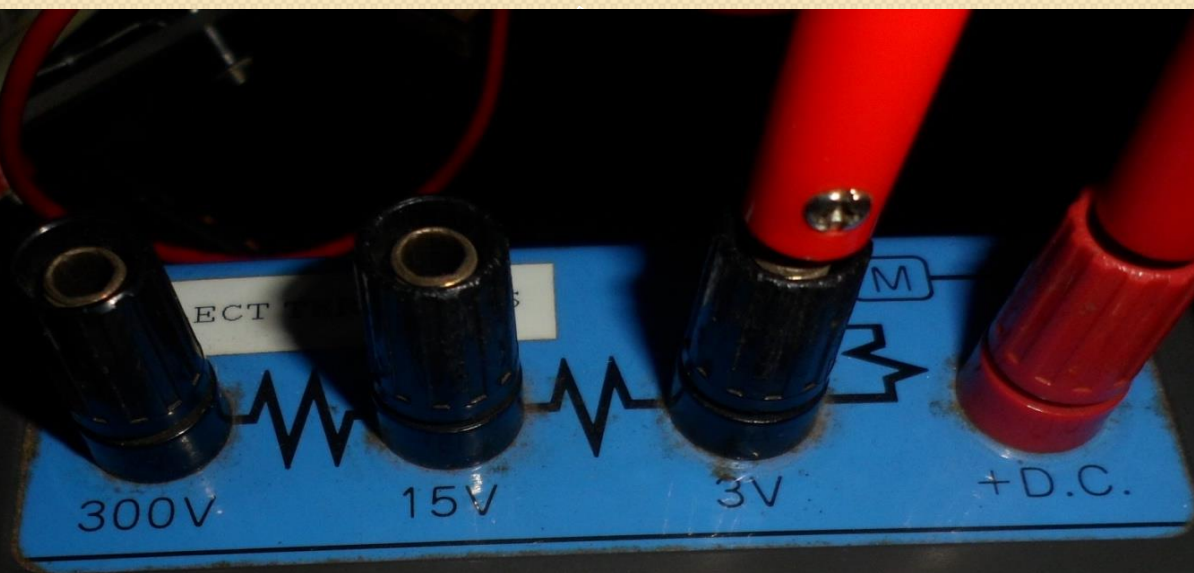




1.4V

Block Diagram of Circuit

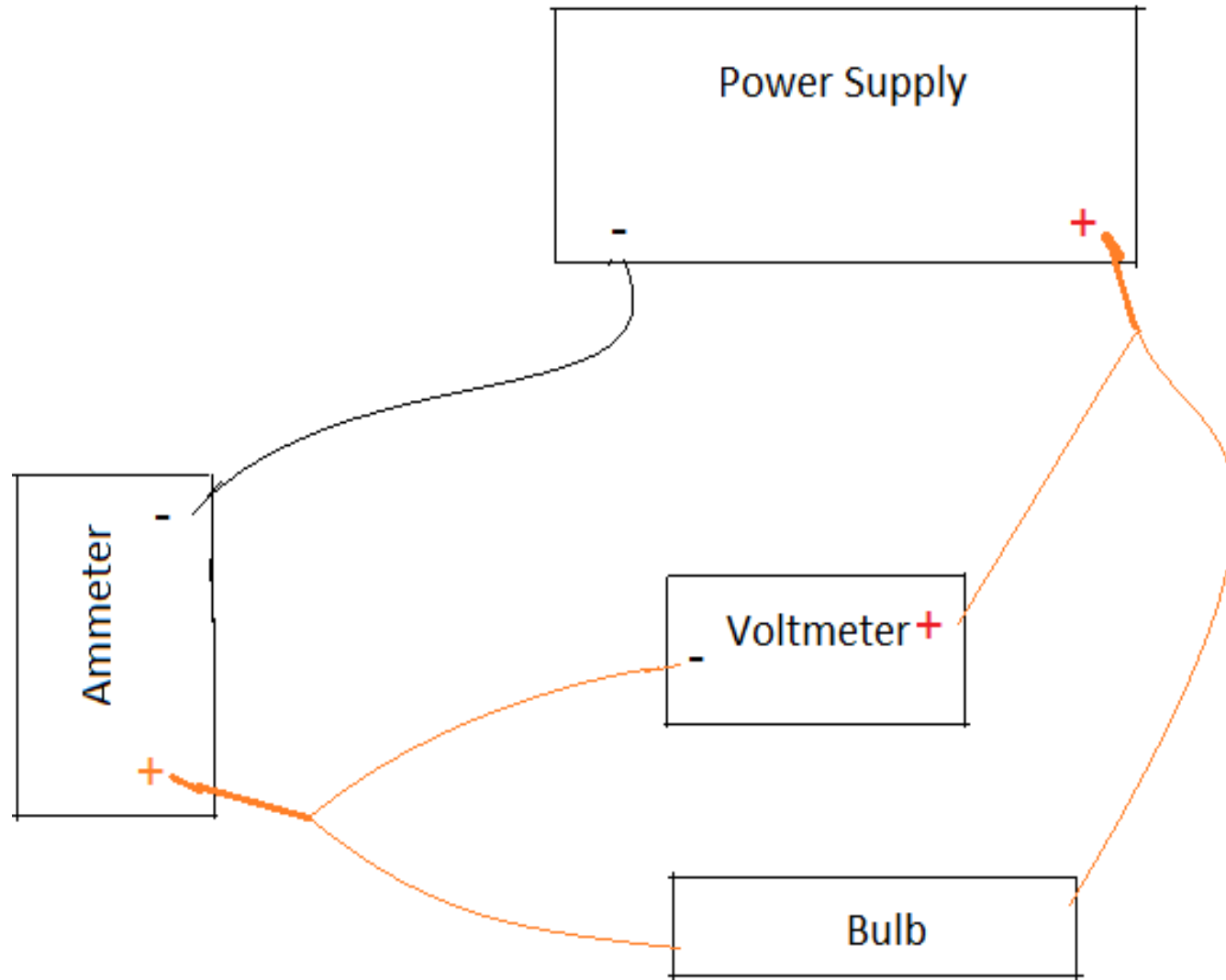

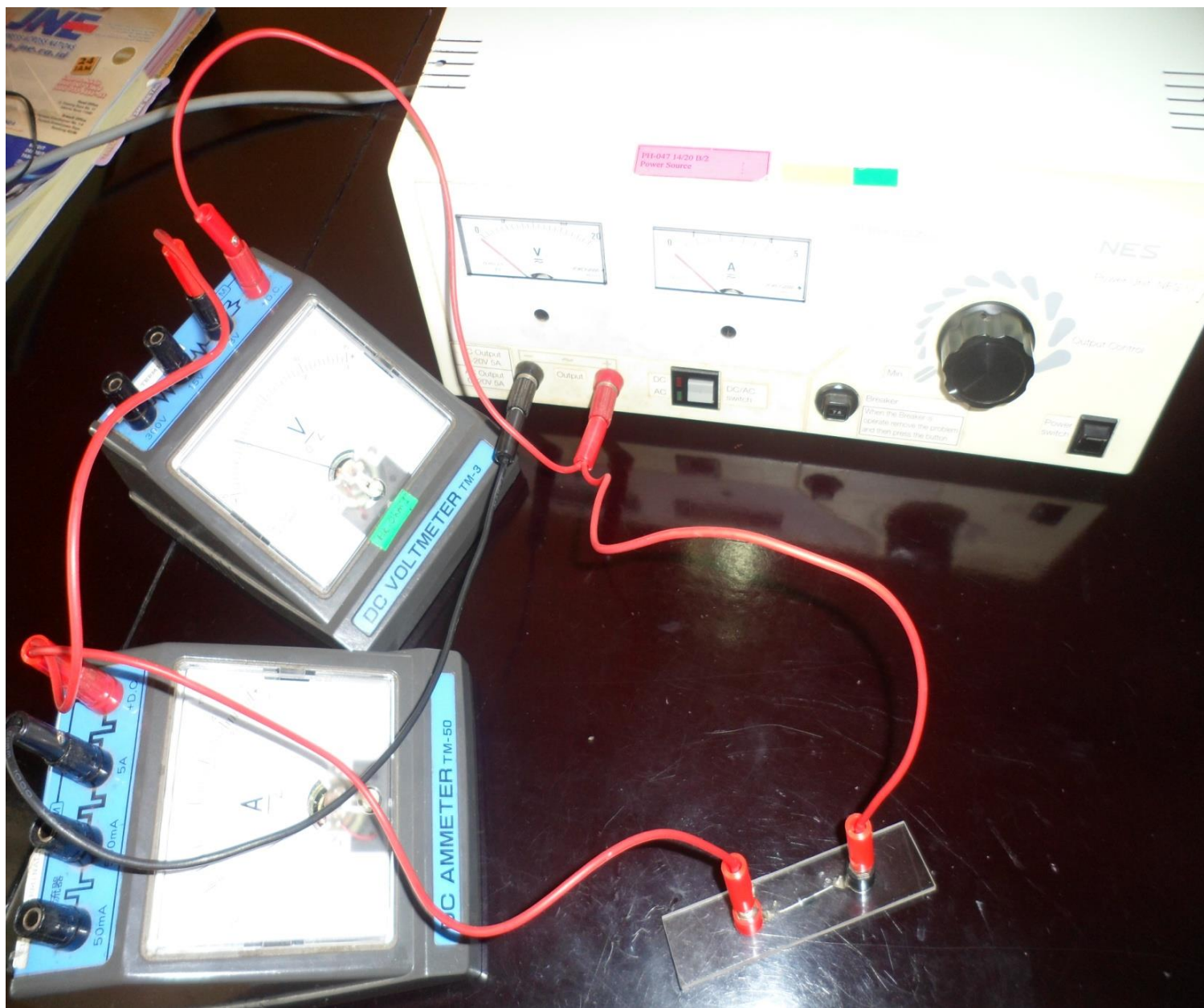

Errors


- ❑ In reality, the data we get is not the same as what we get in theory.

Why?

- ❑ Because **there are sources of error in every aspect**, which make our **numbers imperfect**. For example:
 - personal error
 - Zero error
 - Instrumental error etc.

Voltage versus current graph for the bulb in range of (0- 0.4V)

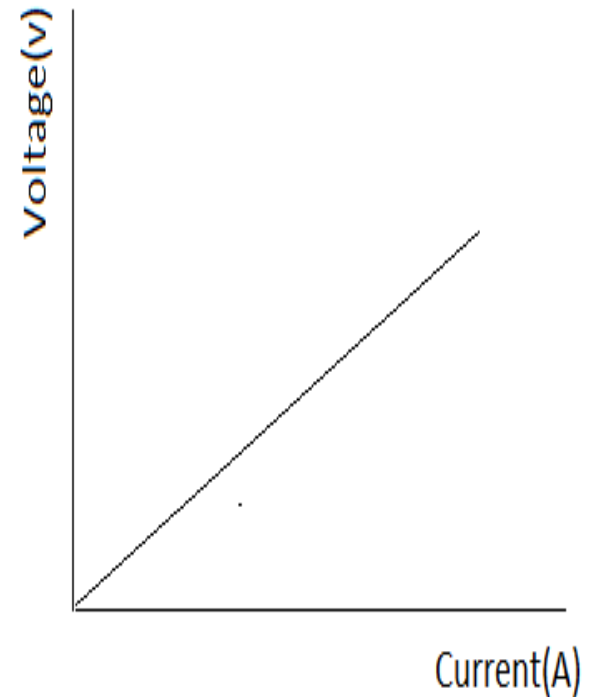- ❑ The graph is **straight line** passing through origin.
- slop is **constant**
- **Slope = Electric resistance**
- In this range, the resistance of the bulb is **constant**
- Devices with constant resistance are called **Ohmic devices**



Conclusion of Experiment A (Ohm's Law)

- Current in ohmic device is directly proportional to voltage across the ends of the device.

$$V \propto I$$

$$V = RI$$


Where: **V** is potential difference (voltage)

I is electric current

R is electrical resistance and **constant**

Voltage versus current graph for Diode

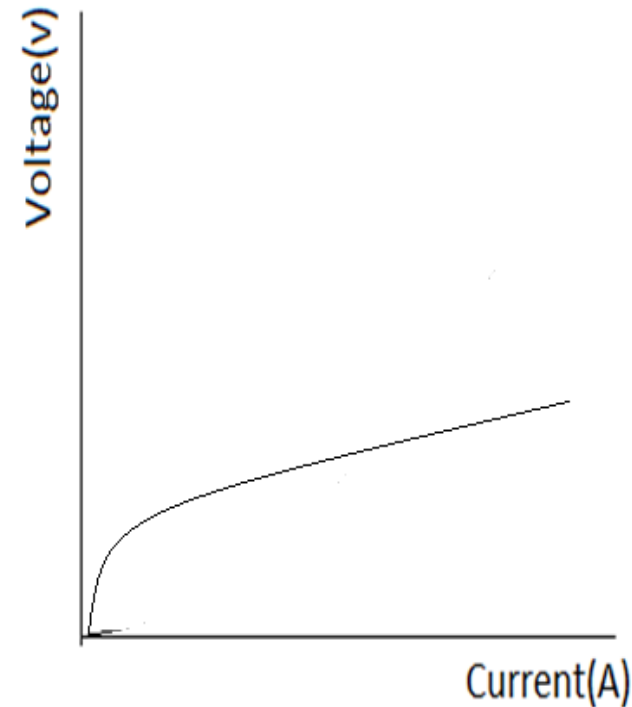- In this case V versus I graph is not a straight line, but **curve**.
- The Slope is **not constant**
- so...resistance of diode is **not constant**.
- Diode is non-ohmic device
- **Non ohmic device does not obey ohm's law**





Tes

waktu **20** menit